

Solution


Q.1) Ampere's Law:  $H_m l_m + H_g l_g = 0 \dots (1)$

Flux:  $\Phi_m = \Phi_g \Rightarrow B_m A_m = B_g A_g$

$A_m = A_g \Rightarrow B_m = B_g \dots (2)$

Combine (1) and (2)  $\Rightarrow$   $B_m = -\frac{l_m}{l_g} \mu_0 H_m$

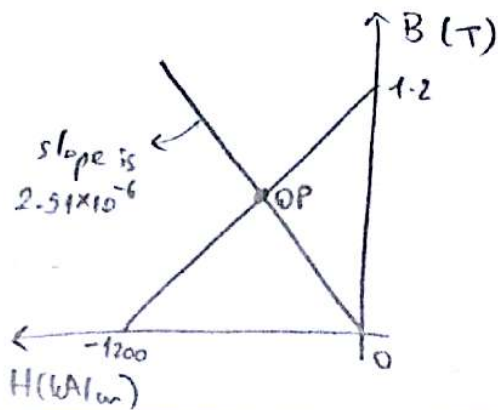Substitute:  $B_m = -2.51 \times 10^{-6} H_m \rightarrow$  Load line equation.



b) Magnet characteristics:  $B_m = B_r + m H_m$  where  $m$  is the slope.

$B_r = 1.2 \text{ T}$

Use  $H_m = -1200 \text{ kA/m}$  point.  $\Rightarrow 0 = 1.2 - m \times 1200 \times 10^3$

$\Rightarrow m = 10^{-6} \Rightarrow$  Magnet char:  $B_m = 1.2 + 10^{-6} H_m$

To find the operating point (OP), use the intersection of the two lines:

$-2.51 \times 10^{-6} H_m = 1.2 + 10^{-6} H_m \Rightarrow H_m = -342 \text{ kA/m}$

$\Rightarrow B_m = -2.51 \times 10^{-6} H_m = 0.858 \text{ T.}$


$OP = (0.858 \text{ T}, -342 \text{ kA/m})$

c)  $EP = B_m \times H_m = (1.2 + 10^{-6} H_m) \times H_m = 1.2 H_m + 10^{-6} H_m^2$

$\frac{\partial(EP)}{\partial(H_m)} = 0 \text{ @ MEP} \Rightarrow 1.2 + 2 \times 10^{-6} H_m = 0 \Rightarrow H_m = -600 \text{ kA/m}$   
 $B_m = 0.6 \text{ T}$  } @ MEP operating point.

$MEP = (0.6 \text{ T}) \times (600 \text{ kA/m}) = 360 \text{ kJ/m}^3$

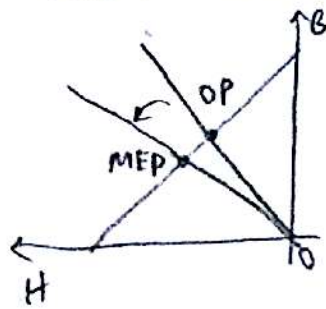- d) OP :  $B = 0.858 \text{ T}$   
MEP OP :  $B = 0.6 \text{ T}$




As shown on the figure, the load line should be shifted down such that it intersects with the magnet characteristics at MEP operating point.

$$B_m = -\frac{l_m}{l_g} \mu_0 H_m$$

To do so, by looking at the equation above;

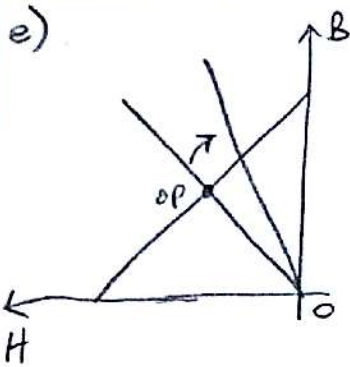- $l_m$  can be decreased
- $l_g$  can be increased



By looking at the equation in part (d), increasing  $l_m$  will shift the load line up as shown on the left. The operating point will move further away from MEP.

- f) Since the core is infinitely permeable, the reluctance will be zero. The magnetic circuit will be as if it is short circuited.

$$B_m = B_r = 1.2 \text{ T} //$$

$$H_m = 0 //$$

- g) As the two magnets are in series and there is no air gap, the same phenomena will occur as in part (f).

$$B_m = 1.2 \text{ T} //$$

$$H_m = 0 //$$

4.2) a)  $N_1 = 60$  turns  
 $N_2 = 120$  turns

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{1}{2} \Rightarrow \text{step-up transformer.}$$

b) Since the secondary terminals are open circuited, the excitation current will only be composed of magnetizing current. Operating point is the saturation point:  $H = 200 \text{ A/m}$ .

$$N_1 I_1 = H l \rightarrow I_1 = \frac{200 \times 0.6}{60} = 2 \text{ Amps}$$

For AC excitation, if the transformer will not be saturated, the current found above should be the peak current.

$$I_{\text{rms}} = \frac{2}{\sqrt{2}} = \sqrt{2} \text{ Amps}$$

c) At saturation point,  $B = 1 \text{ Tesla}$ .

$$E_2 = 4.44 N_2 f B A$$

$$E_2 = 4.44 \times 120 \times 50 \times 1 \times 86 \times 10^{-4}$$

$$E_2 = 230 \text{ V}_{\text{rms}}$$


$$e_2(t) = 230\sqrt{2} \cdot \sin(2\pi 50t) \text{ V}$$

d) Alternatives

- Increase number of turns ( $N_2$ ): More copper loss, more cost (copper)
- Increase frequency ( $f$ ): Hard to implement since system frequency is fixed.
- Increase core area: More cost (core), more core loss
- Use another material with higher  $B_{\text{sat}}$ : Cost.

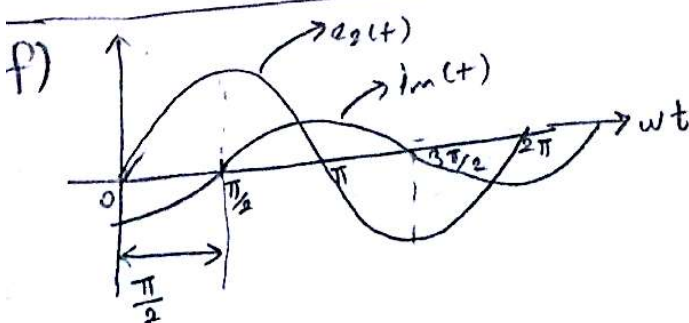e)  $I_m = \sqrt{2} \text{ A}_{\text{rms}}$  (already found)

$$i_m(t) = 2 \cdot \sin(2\pi f t - \pi/2)$$



The phase difference is  $90^\circ$ . It is due to Faraday's Law:  $e = N \frac{d\phi}{dt}$

The magnetization demand of a transformer is purely inductive. Flux (also MMF) and voltage are  $90^\circ$  apart because of the derivative.

This situation can also be interpreted as the reactive power demand of the transformer. (2)




g) No hysteresis loop  $\Rightarrow$  No hysteresis loss.  
It does not mean the core loss is zero. There may still be eddy current loss.

### Q.3) Part I

a)  $I_{\text{rated}} = \frac{P_{\text{rated}}}{V_{2\text{rated}}} = \frac{10 \text{ kVA}}{440 \text{ V}} = 22.7 \text{ A (secondary)}$
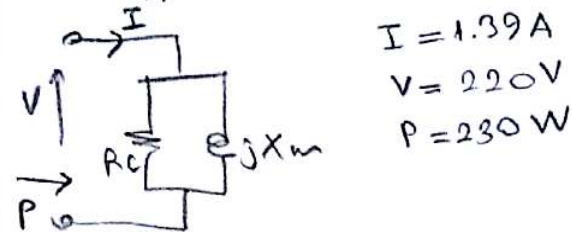
### b) Open circuit test

- There is no current on the secondary
- The impedance of parallel branch is assumed to be much higher.
- Copper loss resistances and leakage reactances can be neglected.



$I = 1.39 \text{ A}$   
 $V = 220 \text{ V}$   
 $P = 230 \text{ W}$

$$R_c = \frac{V^2}{P} = 210 \Omega //$$


$$S = VI = 305.8 \text{ VA}$$

$$Q = \sqrt{S^2 - P^2} = 201.5 \text{ VAR}$$

$$X_m = \frac{V^2}{Q} = 240 \Omega //$$
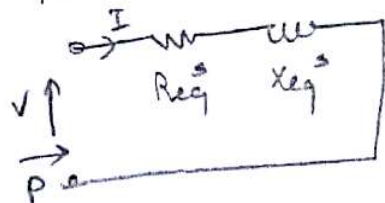
### Short circuit test

- As the primary terminals are short circuited, the impedance of the parallel branch can be neglected.



The test is applied from secondary. The results will be "referred results".

$I = 22.7 \text{ A}$   
 $V = 17.7 \text{ V}$   
 $P = 257 \text{ W}$

$$R_{eq}^s = \frac{P}{I^2} = 0.5 \Omega$$

$$|Z_{eq}^s| = \frac{V}{I} = 0.78 \Omega$$

$$X_{eq}^s = \sqrt{|Z_{eq}^s|^2 - R_{eq}^s{}^2} = 0.6 \Omega$$

### On the primary side:

$$R_{eq} = (N_1/N_2)^2 R_{eq}^s = 0.125 \Omega$$


$$X_{eq} = (N_1/N_2)^2 X_{eq}^s = 0.15 \Omega$$

Assume that  $R_1 = R_2'$  and  $X_1 = X_2'$


$$\Rightarrow R_1 = 62.5 \text{ m}\Omega, R_2 = 0.25 \Omega$$

$$X_1 = 75 \text{ m}\Omega, X_2 = 0.3 \Omega$$

### Equivalent circuit:

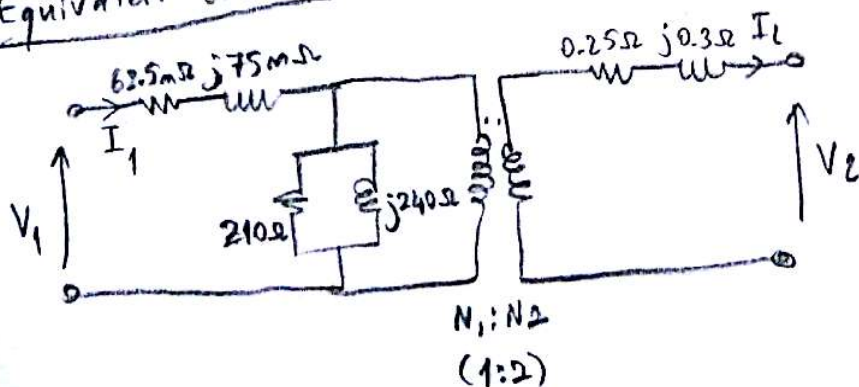

### Part II

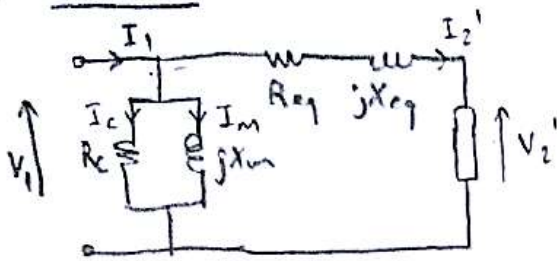

Load: 10 kVA @ 1.0 pf  $\Rightarrow 10 \text{ kW} = P_{out}$

$V_2 = 440 \text{ V} \Rightarrow V_2' = 220 \text{ V}$  (take as the reference phasor)

$I_2' = \frac{P_{out}}{V_2'} = 45.5 \text{ A}$  (in-phase with the secondary voltage,  $V_2'$ )

$$\vec{V}_1 = \vec{V}_2' + \vec{I}_2' \vec{Z}_{eq} \text{ where } \vec{Z}_{eq} = R_{eq} + jX_{eq} = 0.125 + j0.15$$

$$\Rightarrow \vec{V}_1 = 220 + 5.69 + j6.83 = 225.69 + j6.83 = 225.8 \angle 1.7^\circ$$

$$\Rightarrow \boxed{V_1 = 225.8 \text{ V}}$$

$$\vec{I}_c = \frac{\vec{V}_1}{R_c} = \frac{225.8 \angle 1.7^\circ}{210} = 1.08 \angle 1.7^\circ \text{ A}$$

$$\vec{I}_m = \frac{\vec{V}_1}{jX_m} = \frac{225.8 \angle 1.7^\circ}{240 \angle 90^\circ} = 0.94 \angle -88.3^\circ \text{ A}$$


$$\vec{I}_2' = I_2' = 45.5 \angle 0^\circ \text{ A}$$

$$\Rightarrow \vec{I}_1 = \vec{I}_2' + \vec{I}_c + \vec{I}_m = 45.5 + 1.08 + j0.03 + 0.03 - j0.94 = 46.61 - j0.97$$

$$\Rightarrow \vec{I}_1 = 46.62 \angle -1.2^\circ$$

$$\Rightarrow \boxed{I_1 = 46.62 \text{ A}}$$

### Part III

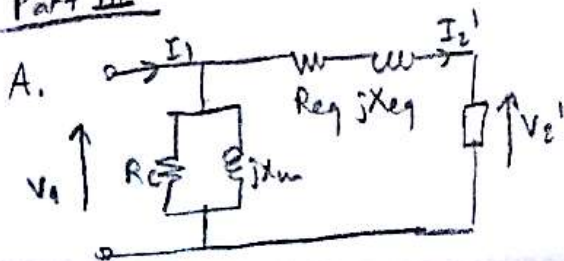

Load: 8 kVA @ 1.0 pf  $\Rightarrow 8 \text{ kW} = P_{out}$

$V_2 = 440 \text{ V} \Rightarrow V_2' = 220 \text{ V}$

$I_2' = \frac{P_{out}}{V_2'} = 36.4 \text{ A}$

$$\vec{V}_1 = \vec{V}_2' + \vec{I}_2' \vec{Z}_{eq}$$

$$\vec{V}_1 = 220 + (36.4 \angle 0^\circ)(0.195 \angle 50^\circ) = 220 + 4.56 + j5.44 = 224.6 \angle 1.39^\circ$$

$$\Rightarrow \boxed{V_1 = 224.6 \text{ V}}$$

$$P_{in} = P_{out} + P_{loss}, P_{loss} = \frac{V_1^2}{R_c} + (I_2')^2 R_{eq} = \frac{(224.6)^2}{210} + (36.4)^2 \times 0.125 = 406 \text{ W}$$

$$\Rightarrow \boxed{P_{in} = 8406 \text{ W}}$$



### Part III

B. Load: 8 kW, 0.8 pf lagging. (Inductive Load)

$$\vec{V}_2' = 220 \text{ V (reference phasor)}$$

$$I_2' = \frac{S_2}{V_2'} = \frac{10 \text{ kVA}}{220 \text{ V}} = 45.45 \text{ A} \Rightarrow \vec{I}_2' = 45.45 \angle -37^\circ \Rightarrow \text{due to lagging pf}$$

$$\vec{V}_1 = \vec{V}_2' + \vec{I}_2' \vec{Z}_{eq}$$

$$\vec{V}_1 = 220 + (45.45 \angle -37^\circ)(0.195 \angle 50^\circ) = 220 + 8.9 \angle 13^\circ = 228.7 + j2 \text{ V}$$

$$\Rightarrow \vec{V}_1 = 228.7 \angle 0.5^\circ \Rightarrow \boxed{V_1 \approx 229 \text{ V}}$$

$$P_{in} = P_{out} + P_{loss}, P_{loss} = \frac{V_1^2}{R_c} + (I_2')^2 R_{eq} = \frac{(229)^2}{210} + (45.45)^2 \times 0.125$$

$$\Rightarrow P_{loss} = 508 \text{ W}$$

$$\Rightarrow \boxed{P_{in} = 8508 \text{ W}}$$

C. Load: 8 kW, 0.8 pf leading (capacitive load)

$$\vec{V}_2' = 220 \text{ V (reference)}$$

$$I_2' = \frac{S_2}{V_2'} = 45.45 \text{ A} \Rightarrow \vec{I}_2' = 45.45 \angle 37^\circ \Rightarrow \text{due to leading pf.}$$

$$\vec{V}_1 = \vec{V}_2' + \vec{I}_2' \vec{Z}_{eq}$$

$$\vec{V}_1 = 220 + (45.45 \angle 37^\circ)(0.195 \angle 50^\circ) = 220 + 8.9 \angle 87^\circ = 220.5 + j8.9 \text{ V}$$

$$\Rightarrow \vec{V}_1 = 220.7 \angle 2.3^\circ \Rightarrow \boxed{V_1 \approx 221 \text{ V}}$$

$$P_{loss} = \frac{V_1^2}{R_c} + (I_2')^2 R_{eq} = \frac{(221)^2}{210} + (45.45)^2 \times 0.125$$

$$\Rightarrow P_{loss} = 491 \text{ W}$$

$$\Rightarrow \boxed{P_{in} = 8491 \text{ W}}$$

D. Regulation

$$1) \text{ reg} = \frac{224.6 - 220}{220} \times 100 = 2\%$$

$$2) \text{ reg} = \frac{229 - 220}{220} \times 100 = 4\%$$

$$3) \text{ reg} = \frac{221 - 220}{220} \times 100 = 0.5\%$$

Efficiency

$$1) \eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{8000}{8406} \times 100 = 95\%$$

$$2) \eta = \frac{8000}{8508} \times 100 = 94\%$$

$$3) \eta = \frac{8000}{8491} \times 100 = 94.2\%$$

Comment:

- With capacitive load, regulation is best. It does not have to be negative!
- With inductive load, regulation is worst.
- Efficiency is maximum for unity pf because the current required to supply 8 kW is minimum under unity pf condition.  $I^2R$  (copper) losses are minimum.
- In the capacitive load, efficiency is better than inductive load since  $V_1$  is smaller and so that core loss is smaller  $\left(\frac{V_1^2}{R}\right)$ .